

CENG 215 CIRCUITS and ELECTRONICS

Project #1 - A

Task: Write a Python code to simulate the circuit shown below. The circuit contains a special nonlinear diode (called *X-diode*), an inductor, and one capacitor. Node voltages are denoted by $V_c(t)$ and $V_l(t)$ as in the original schematic.

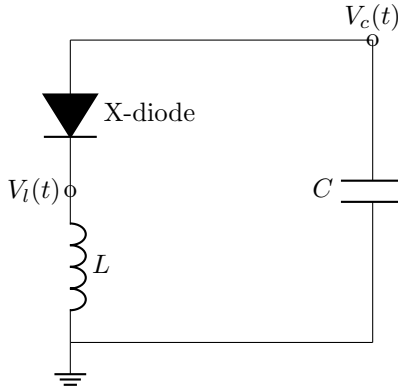


Figure 1: Two-branch circuit: left branch X-diode and inductor in series, right branch capacitor.

X-diode model:

In this project you *must not* use the standard Shockley diode equation. Instead, the diode current--voltage characteristic of the X-diode is given *only* by the measured curve in Fig. 2. This curve is specific to this exam and does not correspond to any standard datasheet model.

According to this V-I characteristics, for example, $v_D \approx 0.25V$ when $0 < i_D < 5mA$, $v_D \approx 0.6V$ when $15 < i_D < 17.5mA$, and so on. Also note that diode does not allow negative currents, meaning that it becomes open circuit when current drops to zero.

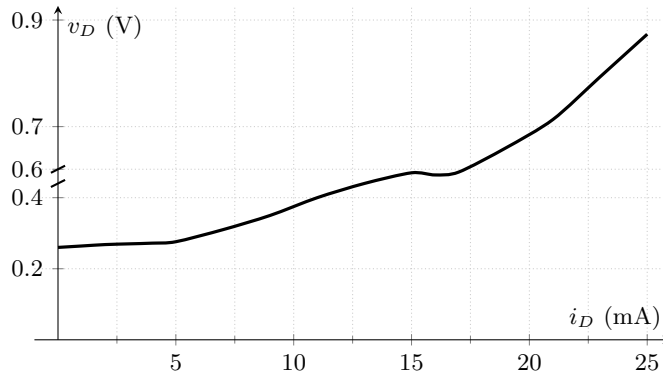


Figure 2: Approximate measured i_D - v_D characteristic of the X-diode.

Important: The vertical axis in Fig. 2 uses a non-uniform scale. The tick labels (0, 0.2, 0.4, 0.6, 0.7, 0.9V) do not correspond to equal spacing in the plot. You must read the curve qualitatively and construct a suitable approximate model (e.g., piecewise linear model) for your simulation.

Simulation tasks:

Write a Python program that:

- a) Approximates the X-diode i_D -- v_D characteristic in Fig. 2 by a suitable analytical or piecewise defined function that you can use in a time-domain circuit simulation (e.g., in a function `v_diode(i)` or `i_diode(v)`). State clearly in your report how you obtained this approximation from the graph.
- b) Simulates the transient behavior of the given circuit assuming that the initial voltage of the capacitor is given as $V_c(0) = 3$ volts. Inductor has no initial energy ($i_l(0) = 0$)
(Use state equations and Euler method for simulation)
- c) Plots $V_c(t)$ and $V_l(t)$ on appropriately scaled axes.
- d) Find out the final value of the capacitor voltage V_c .

What to submit:

At the end of the lab session, submit a brief report (as a Word or PDF document) that includes:

1. Your Python code.
2. Your approximate mathematical model of the X-diode characteristic (derived from Fig. 2).
3. Simulation results: clearly labeled plots of $V_c(t)$ and $V_l(t)$ for both input signals.