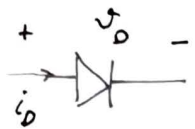


Diode Applications





$$i_D = I_S (e^{v_D/V_{TH}} - 1)$$



$$V_{TH} = \frac{kT}{q} \approx 0.025 \text{ V at room temperature.}$$

$$I_S \approx 10^{-12} \text{ A}$$


Generally modeled as:

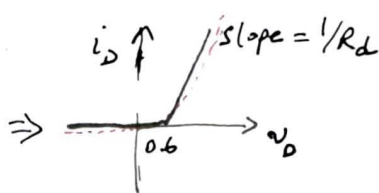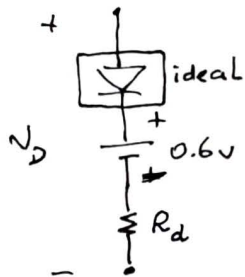

Half-rectifier circuit:

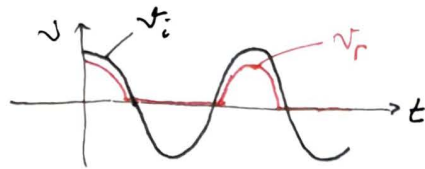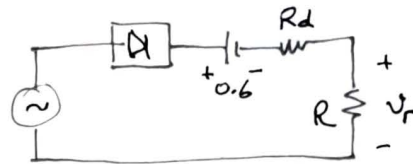


ON case:

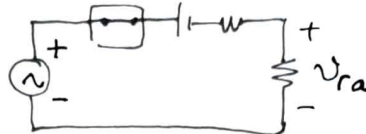


$$v_{ra} = (v_i - 0.6) \frac{R}{R + R_d}$$

OFF case:

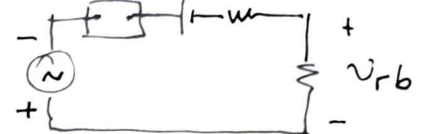

$$v_{rb} = 0$$

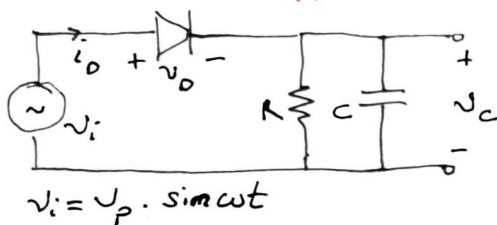* Non-linear analysis with RC (Peak-detector application)




$$i_D = \frac{v_c}{R} + C \frac{dv_c}{dt}$$

$$v_D = v_i - v_c$$

$$i_D = I_S (e^{q(v_i - v_c)/kT} - 1)$$


$$\frac{dv_c}{dt} = -\frac{v_c}{RC} + \frac{I_S}{C} [e^{q(v_i - v_c)/kT} - 1] \quad \text{state equation}$$

Half-wave rectifier (DC supply)

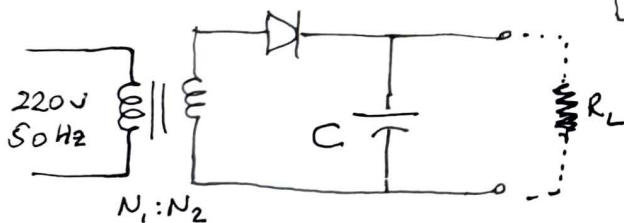

Recall transformers

Full-wave rectifier (DC supply)

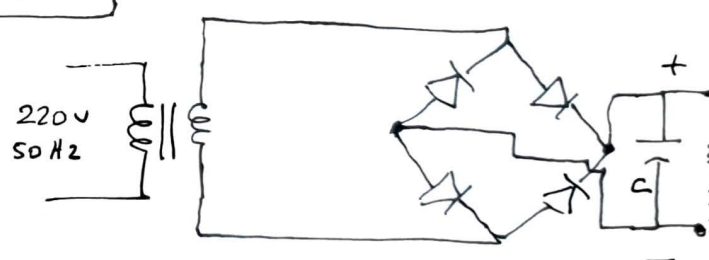

peak-detector.py

- 1) $\sin(50 \text{ Hz})$
- 2) observe the effect of C and R_L
- 3) Try with a variable amplitude sine (can it track the peak?)
- 4) Find the point that it cannot track the peak well by playing with ω , C , R_L parameters.